


## Experiment 1

### Aim:

To verify Superposition Theorem.
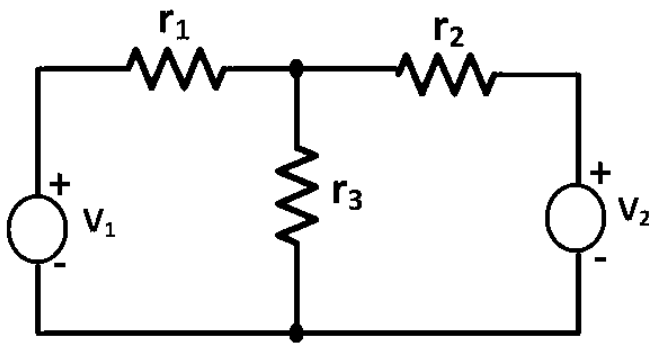
### Theory:

If a number of voltage or current source are acting simultaneously in a linear network, the resultant current in any branch is the algebraic sum of the currents that would be produced in it, when each source acts alone replacing all other independent sources by their internal resistances.



In the given figure apply superposition theorem,

Let us first take the sources V1 alone at first replacing V2 by short circuit. Here,

$$I'_1 = \frac{V_1}{\frac{R_2 * R_3}{R_2 + R_3} + R_1}$$

$$I'_2 = I'_1 * \frac{R_3}{R_2 + R_3}$$

$$I'_3 = I'_1 - I'_2$$

Next, removing V1 by short circuit, let the circuit be energized by V2 only. Then,

$$I''_2 = \frac{V_2}{\frac{R_1 * R_3}{R_1 + R_3} + R_2}$$

$$I''_1 = I''_2 * \frac{R_3}{R_1 + R_3}$$

$$I''_3 = I''_2 - I''_1$$


As per superposition theorem,

$$I_3 = I'_3 + I''_3$$

$$I_2 = I'_2 + I''_2$$

$$I_1 = I'_1 + I''_1$$

## Procedure:

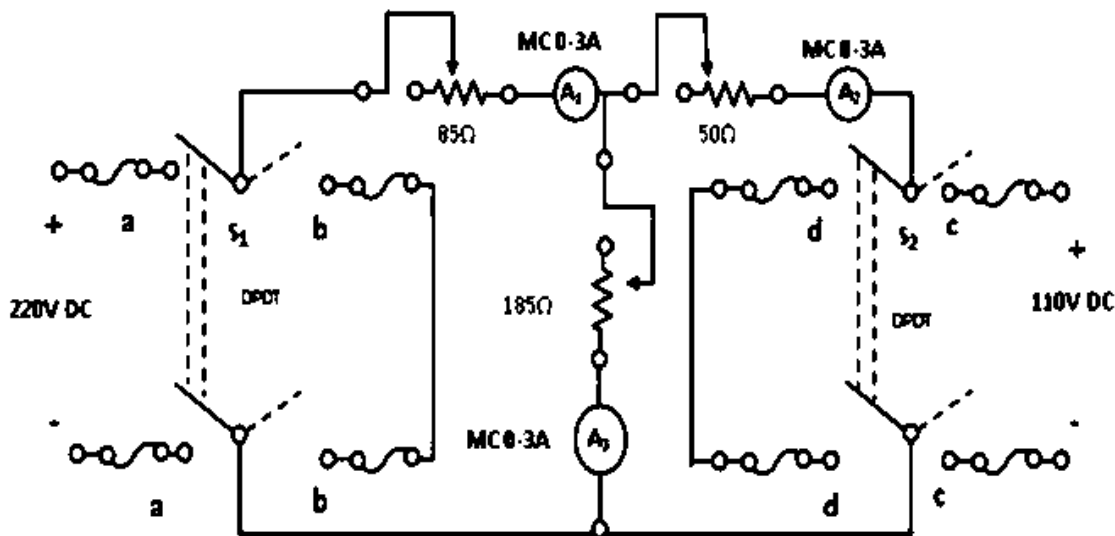

1. Connect the circuit as shown in the diagram, keeping the switches open and resistance at their maximum positions.
2. Set  $S_1$  to position "aa" and  $S_2$  to position "cc" respectively which means both the sources are energized. Note down the current  $I_1$ ,  $I_2$  and  $I_3$  from ammeter  $A_1$ ,  $A_2$  and  $A_3$ .
3. Set  $S_1$  to positions "aa" and  $S_2$  to position "dd" respectively which means the, only 220V source is energized and the terminals of  $S_2$  are shorted. Note down current  $I'_1$ ,  $I'_2$  and  $I'_3$  from the ammeter  $A_1$ ,  $A_2$  and  $A_3$ .
4. Set  $S_1$  to position "bb" and  $S_2$  to position to "cc" respectively. Which means the, only 110V source is energized and the terminals of  $S_1$  are shorted. Note down current  $I''_1$ ,  $I''_2$  and  $I''_3$  from the ammeter  $A_1$ ,  $A_2$  and  $A_3$ .
5. Compare  $I_1$ ,  $I_2$  and  $I_3$  with  $I'_1 + I''_1$ ,  $I'_2 + I''_2$  and  $I'_3 + I''_3$  taking care of signs properly of verify the theorem.
6. Repeat the step (2) to (6) for five different values of resistance for each three rheostats.

## Observations:

Serial no. of Observation	In presence of both $V_1$ and $V_2$			In presence of $V_1$ only			In presence of $V_2$ only		
	Brach current $I_1$ (in amps)	Brach current $I_2$ (in amps)	Brach current $I_3$ (in amps)	Brach current $I_1$ (in amps)	Brach current $I_2$ (in amps)	Brach current $I_3$ (in amps)	Brach current $I_1$ (in amps)	Brach current $I_2$ (in amps)	Brach current $I_3$ (in amps)
1st	0.39032	-0.10645	0.28387	0.56774	-0.35484	0.21290	-0.17742	0.24839	0.070968
2nd	0.62857	-0.23571	0.39286	0.94286	-0.62857	0.31429	-0.31429	0.39286	0.078571
3rd	0.73333	-0.36667	0.36667	1.2222	-0.97778	0.24444	-0.48889	0.61111	0.12222
4th	1.1000	0.0000	1.1000	1.4667	-0.73333	0.73333	-0.36667	0.73333	0.36667
5th	0.21064	-0.046809	0.16383	0.37447	-0.32766	0.046809	-0.16383	0.28085	0.11702

## Calculations:

### For 1<sup>st</sup> Observations:

$$V_1 = 220V, V_2 = 110V, R_1 = 200 \text{ ohm}, R_2 = 300 \text{ ohm}, R_3 = 500 \text{ ohm}$$

Case I: When both sources are present, (Using Kirchhoff Voltage Law)

$$-V_1 + I_1 R_1 - I_2 R_2 + V_2 = 0 \dots (i)$$

$$-V_1 + I_1 R_1 + I_3 R_3 = 0 \dots (ii)$$

$$-V_2 + I_2 R_2 + I_3 R_3 = 0 \dots (iii)$$

Solving (i),(ii) and (iii) and putting values we get,

$$I_1 = 0.3903225806 \text{ A}$$

$$I_2 = -0.1064516129 \text{ A}$$

$$I_3 = 0.2838709677 \text{ A}$$

Case II: When  $V_2$  is short,

$$I'_1 = \frac{V_1}{\frac{R_2 * R_3}{R_2 + R_3} + R_1} = \frac{220}{\frac{300 * 500}{300 + 500} + 200} = 0.5677419355 \text{ A}$$

$$I'_2 = I'_1 * \frac{R_3}{R_2 + R_3} = 0.5677419355 * \frac{500}{300 + 500} = 0.3548387097 \text{ A } (-ve \text{ direction})$$

$$I'_3 = I'_1 - I'_2 = 0.5677419355 - 0.3548387097 = 0.2129032258 \text{ A}$$

Case III: When  $V_3$  is short,

$$I''_2 = \frac{V_2}{\frac{R_1 * R_3}{R_1 + R_3} + R_2} = \frac{110}{\frac{200 * 500}{200 + 500} + 300} = 0.2483870968 \text{ A}$$

$$I''_1 = I''_2 * \frac{R_3}{R_1 + R_3} = 0.2483870968 * \frac{500}{200 + 500} = 0.1774193549 \text{ A } (-ve \text{ direction})$$

$$I''_3 = I''_2 - I''_1 = 0.2483870968 - 0.1774193549 = 0.0709677419 \text{ A}$$

According to Superposition Theorem,

$$I_3 = I'_3 + I''_3$$

$$I_2 = I'_2 + I''_2$$

$$I_1 = I'_1 + I''_1$$

$$I'_1 + I''_1 = 0.5677419355 - 0.1774193549 = 0.3903225806 \text{ A} = I_1$$

$$I'_2 + I''_2 = -0.3548387097 + 0.2483870968 = -0.1064516129 \text{ A} = I_2$$

$$I'_3 + I''_3 = 0.2129032258 + 0.0709677419 = 0.2838709677 \text{ A} = I_3$$

Superposition Theorem is verified in 1<sup>st</sup> observation.

1<sup>st</sup> observation is verified and similarly we can verify rest of the observations similar way,

**2<sup>nd</sup> observation:**

$$I_1' + I_1'' = 0.94286 - 0.31429 = 0.62857 A = I_1$$

$$I_2' + I_2'' = -0.62857 + 0.39286 = -0.23571 A = I_2$$

$$I_3' + I_3'' = 0.31429 + 0.078571 = 0.39286 A = I_3$$

**3<sup>rd</sup> observation:**

$$I_1' + I_1'' = 1.22222 - 0.48889 = 0.73333 A = I_1$$

$$I_2' + I_2'' = -0.97778 + 0.61111 = -0.36667 A = I_2$$

$$I_3' + I_3'' = 0.24444 + 0.12222 = 0.36667 A = I_3$$

**4<sup>th</sup> observation:**

$$I_1' + I_1'' = 1.46667 - 0.36667 = 1.10000 A = I_1$$

$$I_2' + I_2'' = -0.73333 + 0.73333 = 0.00000 A = I_2$$

$$I_3' + I_3'' = 0.73333 + 0.36667 = 1.10000 A = I_3$$

**5<sup>th</sup> observation:**

$$I_1' + I_1'' = 0.37447 - 0.16383 = 0.21064 A = I_1$$

$$I_2' + I_2'' = -0.32766 + 0.28085 = -0.046809 A = I_2$$

$$I_3' + I_3'' = 0.046809 + 0.11702 = 0.16383 A = I_3$$

**Results:**

We have successfully verified Superposition Theorem.

All of the observations are verified.