

## Experiment VII

### AIM:

Design of Full Subtractor and Adder using 8:1 Multiplexer.


### Theory:

#### Multiplexer:

A multiplexer (MUX) is a combinational circuit with many data inputs and based on control inputs, single data outputs are generated.

For n:1 MUX, n number of input lines are required,  $\log_2 n$  number of control/selection lines are required.

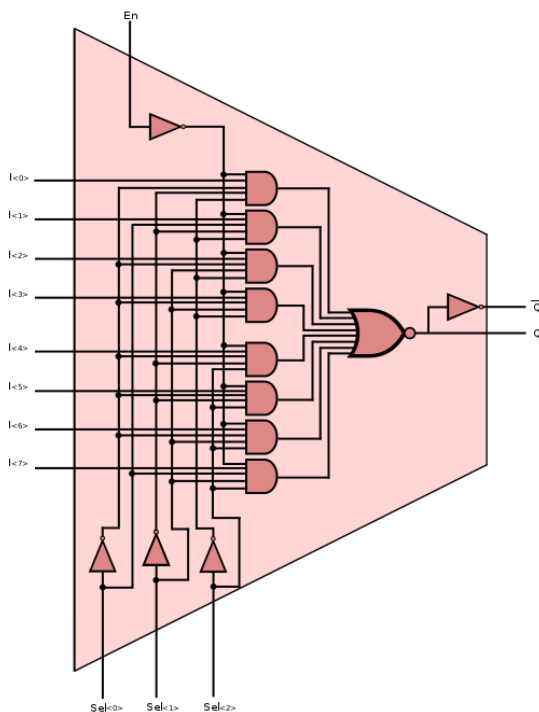For 8:1 MUX, we have 8 input lines and 1 output line with 3 selection lines.



Truth table for 8:1 MUX

INPUTS			Output
S <sub>2</sub>	S <sub>1</sub>	S <sub>0</sub>	Y
0	0	0	A <sub>0</sub>
0	0	1	A <sub>1</sub>
0	1	0	A <sub>2</sub>
0	1	1	A <sub>3</sub>
1	0	0	A <sub>4</sub>
1	0	1	A <sub>5</sub>
1	1	0	A <sub>6</sub>
1	1	1	A <sub>7</sub>

**Full Adder:**

Full adder is developed to overcome the drawback of Half Adder circuit. It can add two one-bit numbers A and B, and carry c.

The full adder is a three input (A, B,  $C_{in}$ ) and two output (Sum, Carry) combinational circuit.

Inputs			Outputs	
A	B	$C_{in}$	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

From here we get,

For Full Adder,

$$\text{Sum}(A, B, C_{in}) = \Sigma(1, 2, 4, 7)$$

$$\text{Carry}(A, B, C_{in}) = \Sigma(3, 5, 6, 7)$$

**Full Subtractor:**

The full subtractor is a combinational circuit with three inputs A, B, C and two output D and  $B_{out}$ . A is the 'minuend', B is 'subtrahend', C is the 'borrow' produced by the previous stage, D is the difference output and  $B_{out}$  is the borrow output.

Inputs			Outputs	
A	B	$\text{Borrow}_{in}$	Diff	Borrow
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

From here we get,


For Full Subtractor,

$$\text{Difference}(A, B, C) = \Sigma(1, 2, 4, 7)$$

$$\text{Borrow}(A, B, C) = \Sigma(1, 2, 3, 7)$$

## Observations:


When  $A = 0$ ,  $B = 0$  and  $C = 0$ :

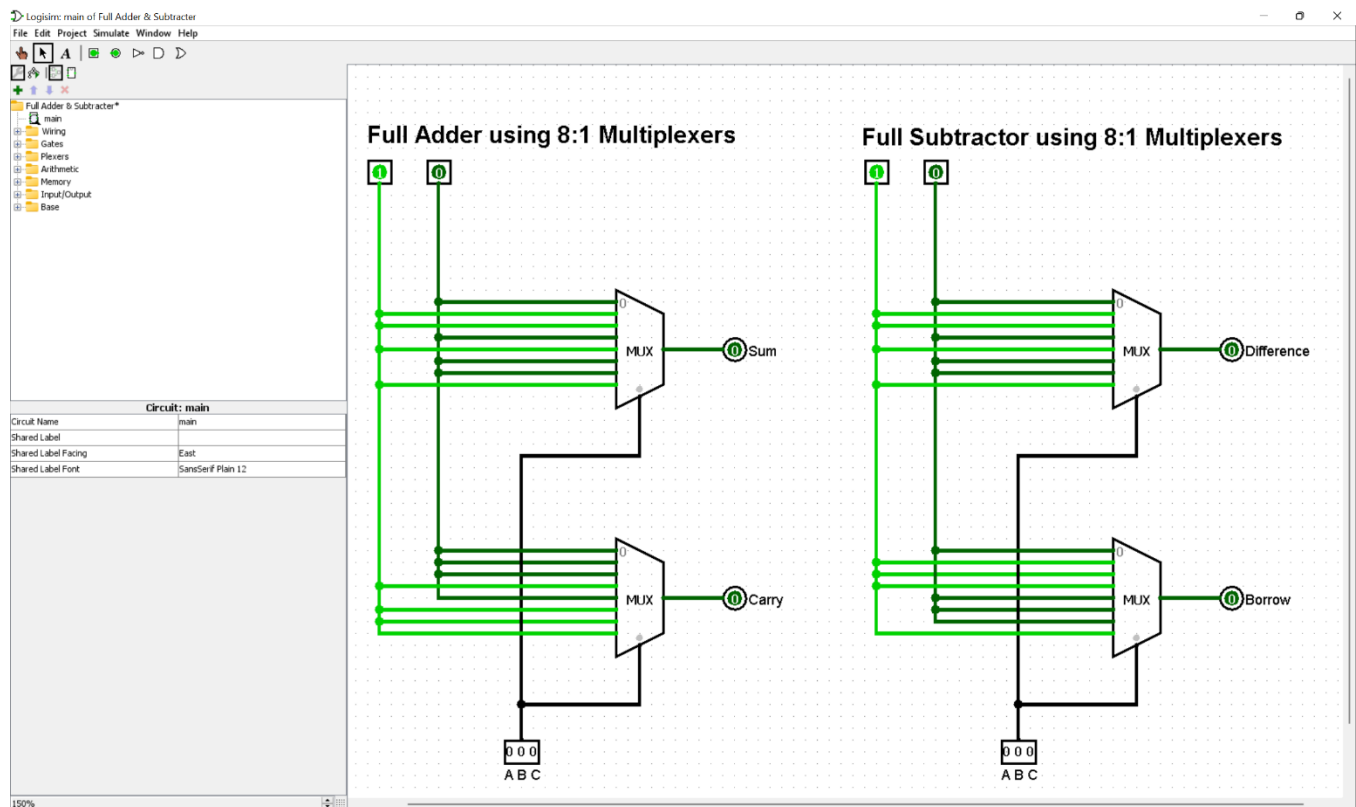

Full Adder: Sum = 0, Carry = 0

Full Subtractor: Difference = 0, Borrow = 0


When  $A = 0$ ,  $B = 0$  and  $C = 1$ :

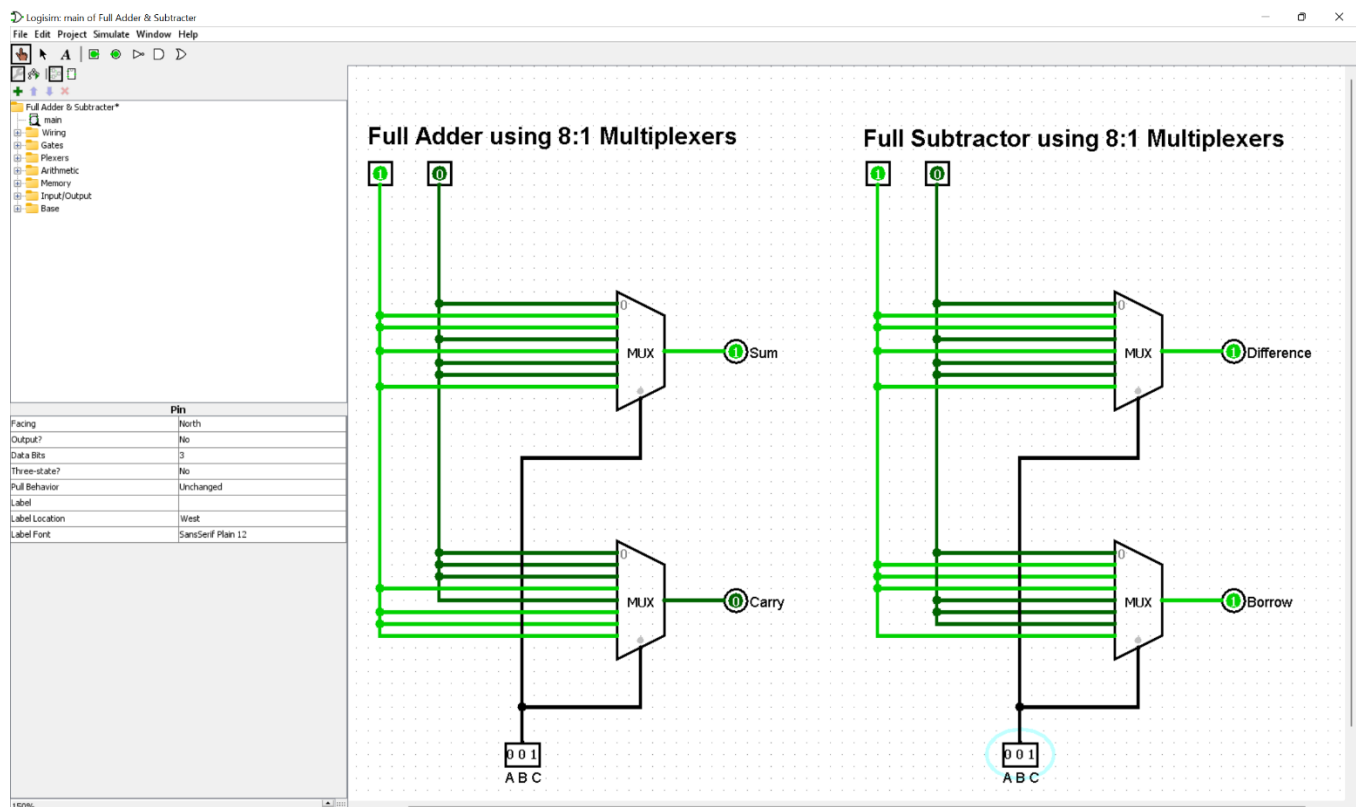

Full Adder: Sum = 1, Carry = 0

Full Subtractor: Difference = 1, Borrow = 1


**When A = 0, B = 1 and C = 0:**

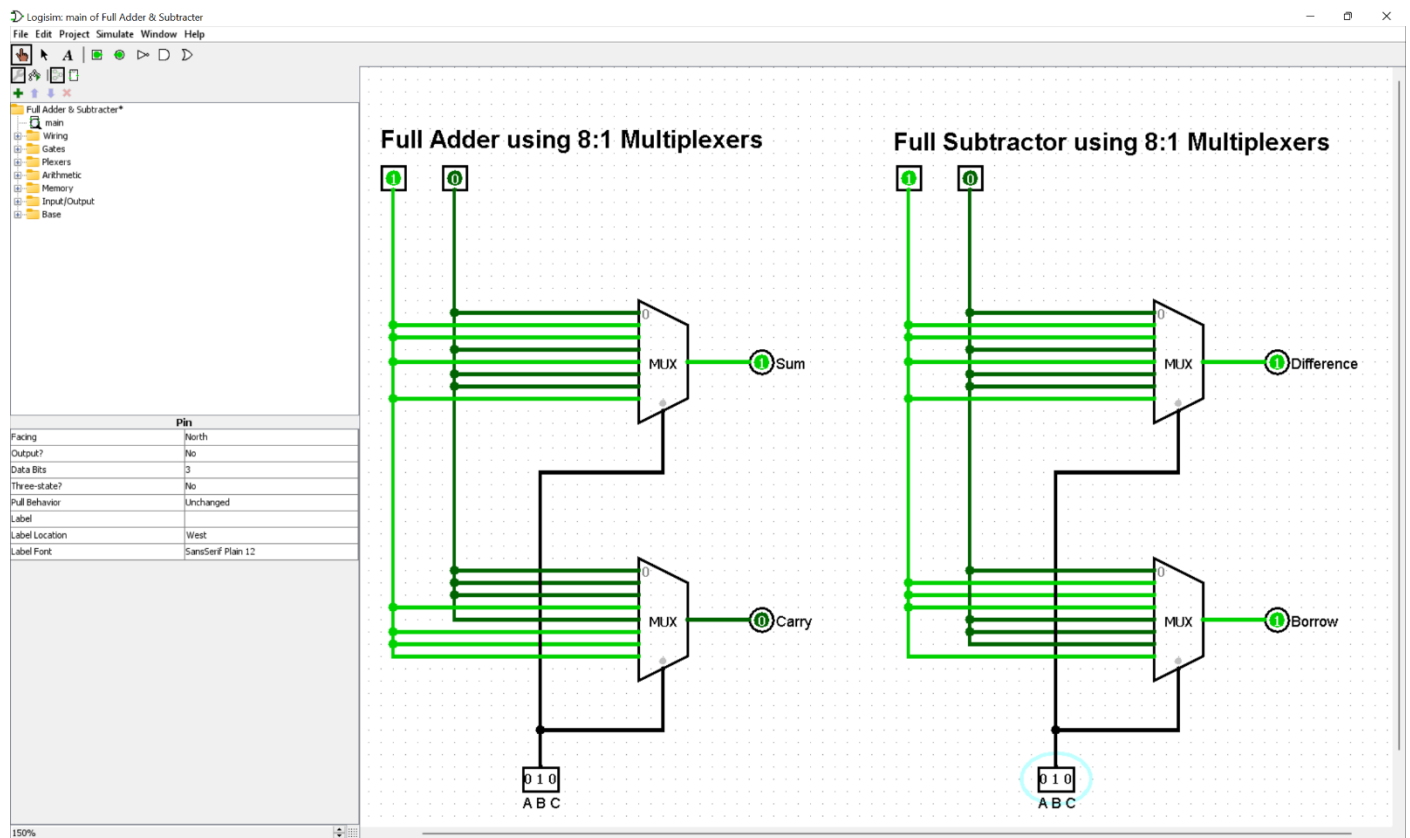

Full Adder: Sum = 1, Carry = 0

Full Subtractor: Difference = 1, Borrow = 1


**When A = 0, B = 1 and C = 1:**

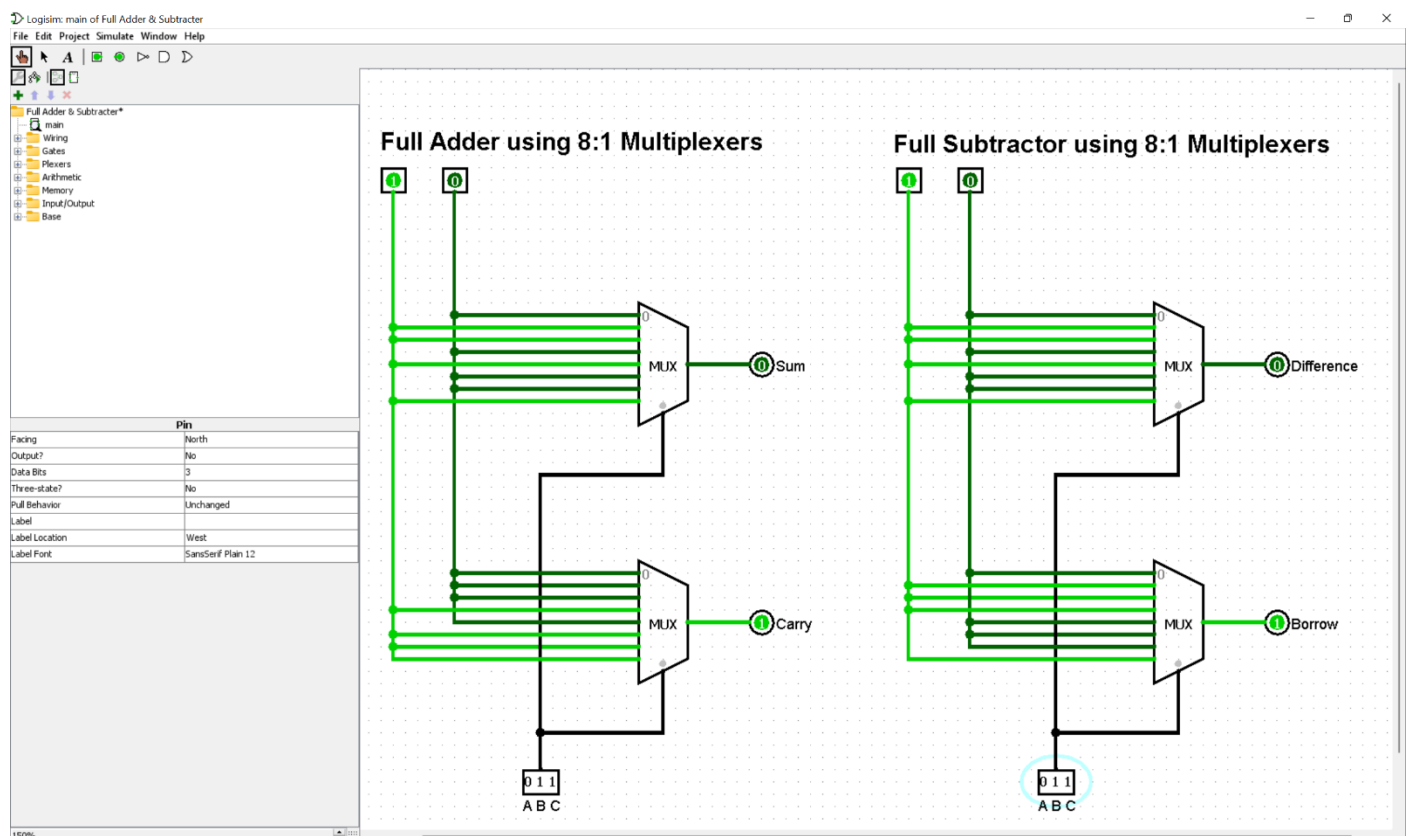

Full Adder: Sum = 0, Carry = 1

Full Subtractor: Difference = 0, Borrow = 1


**When A = 1, B = 0 and C = 0:**

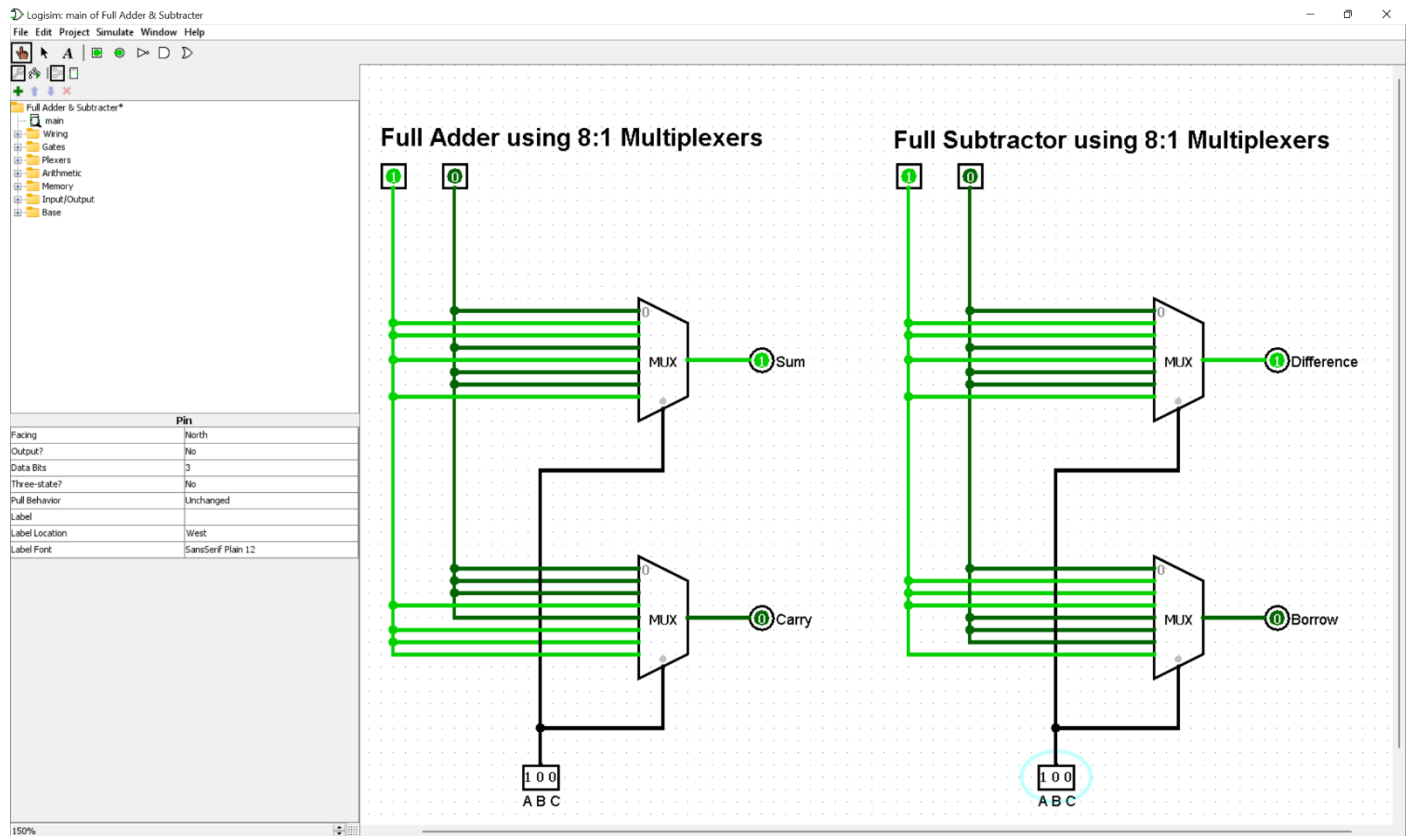

Full Adder: Sum = 1, Carry = 0

Full Subtractor: Difference = 1, Borrow = 0


**When A = 1, B = 0 and C = 1:**

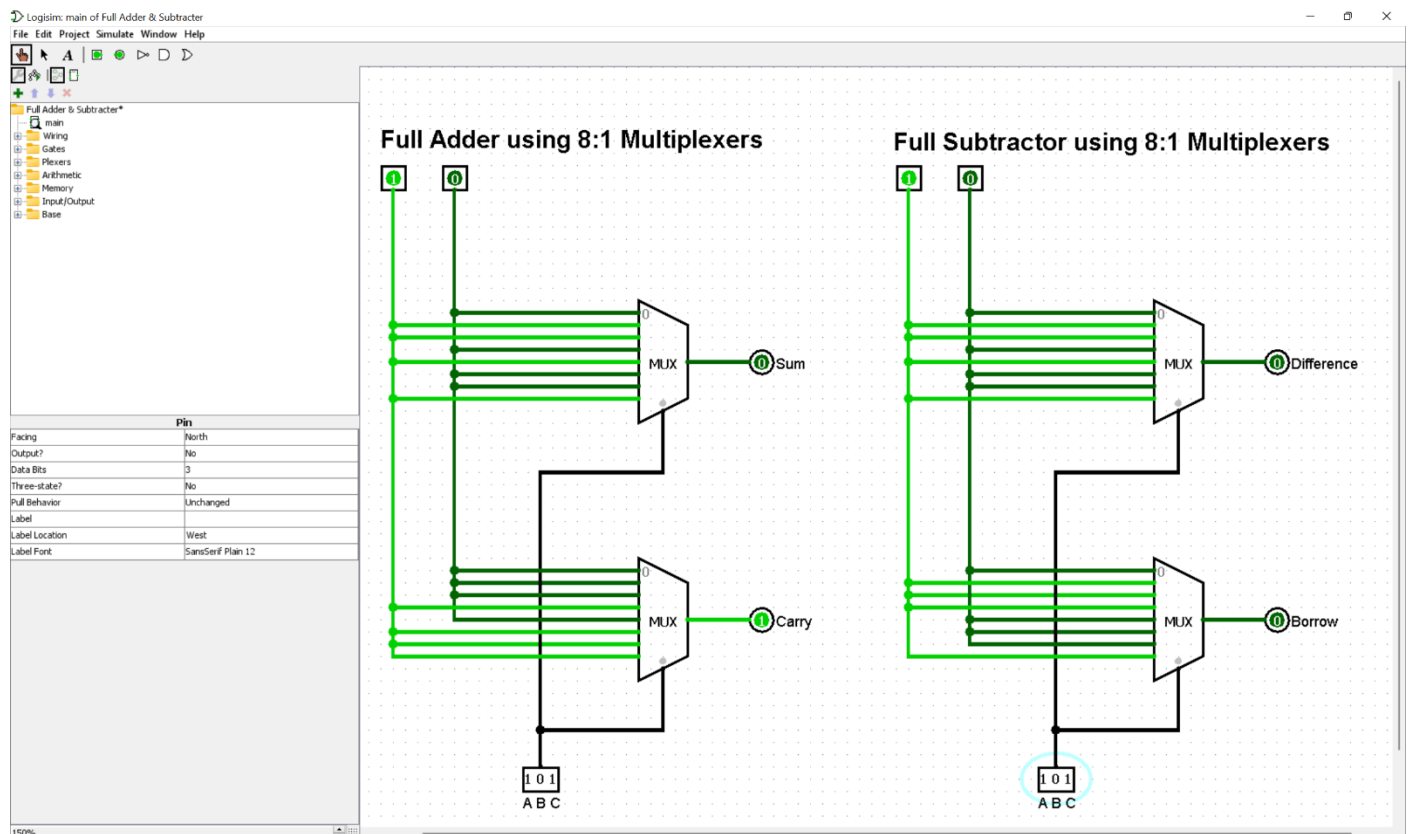

Full Adder: Sum = 0, Carry = 1

Full Subtractor: Difference = 0, Borrow = 0


**When A = 1, B = 1 and C = 0:**

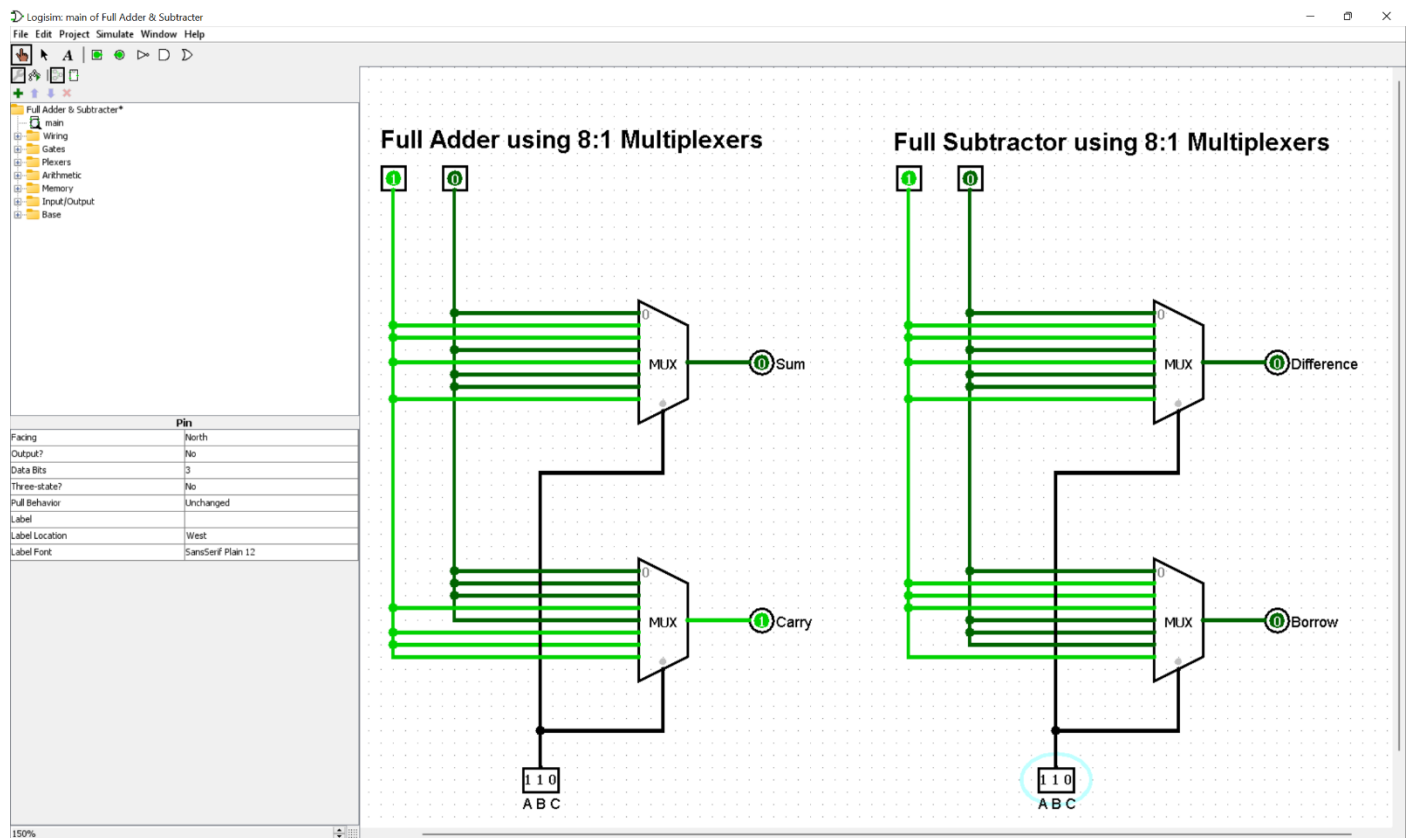

Full Adder: Sum = 0, Carry = 1

Full Subtractor: Difference = 0, Borrow = 0

**When A = 1, B = 1 and C = 1:**

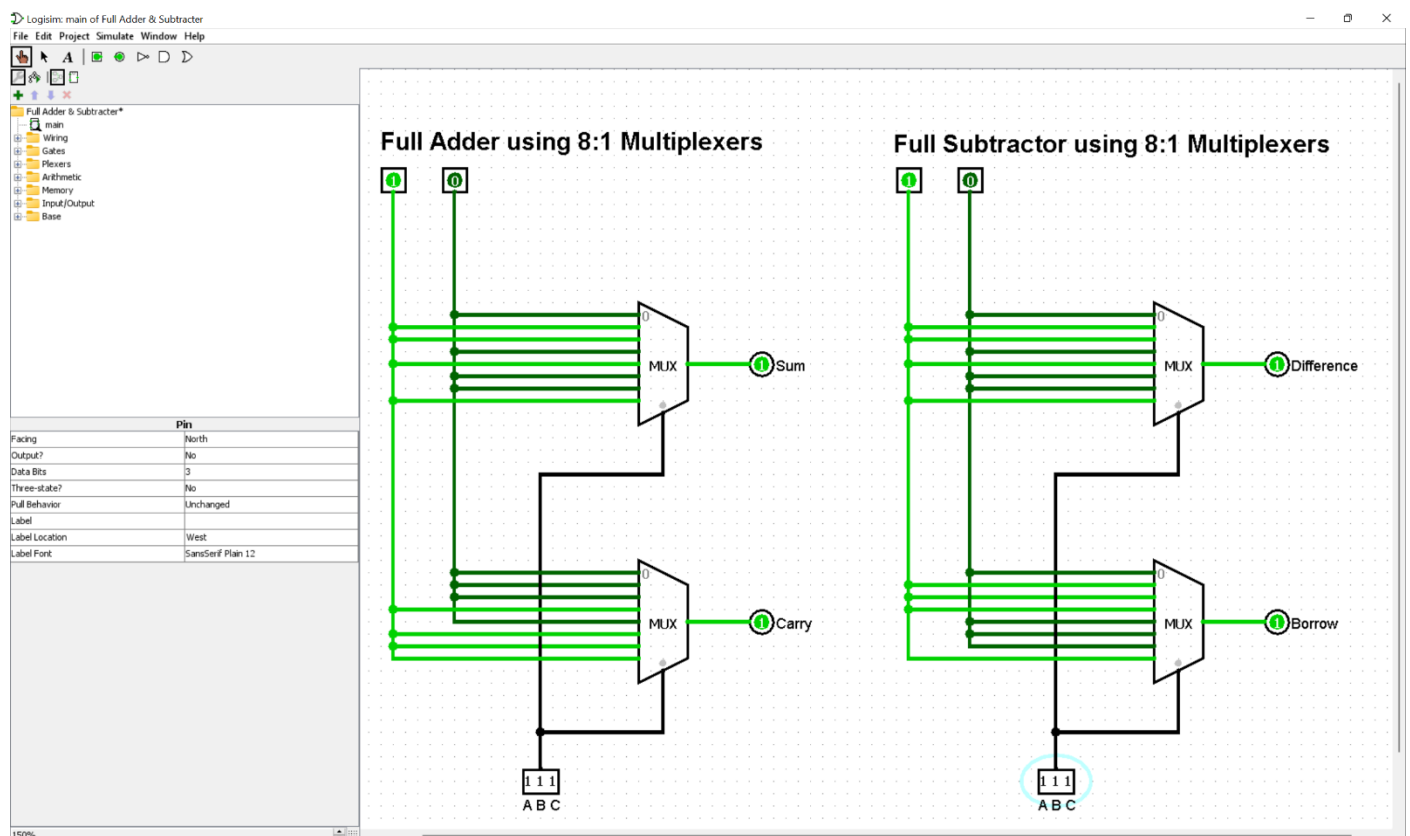

Full Adder: Sum = 1, Carry = 1

Full Subtractor: Difference = 1, Borrow = 1