

Experiment I

AIM:

Design a Voltage Divider Circuit with:

1. $R_1 = R_2$
2. R_1 variable and R_2 fixed.

Theory:

Voltage Divider:

In electronics, a voltage divider (also known as a potential divider) is a passive linear circuit that produces an output voltage (V_{out}) that is a fraction of its input voltage (V_{in}). Voltage division is the result of distributing the input voltage among the components of the divider. A simple example of a voltage divider is two resistors connected in series, with the input voltage applied across the resistor pair and the output voltage emerging from the connection between them.

Circuit Analysis:

Let input AC voltage be V_{in} with frequency ν , Phase 0 degrees and RMS voltage V_{rms}

$$V_{in} = V_{rms}\sqrt{2} \sin(2\pi\nu t + 0) \text{ V} = V_{rms}\sqrt{2} \sin(2\pi\nu t) \text{ V}$$

Current in the circuit,

$$i = \frac{V_{in}}{R_1 + R_2} \text{ A}$$

Voltage across R_1 ,

$$V_{R_1} = \frac{R_1 V_{in}}{R_1 + R_2} \text{ V}$$

Voltage across R_2 ,


$$V_{R_2} = \frac{R_2 V_{in}}{R_1 + R_2} \text{ V}$$

Output Voltage V_{out} ,

$$V_{out} = V_{R_2} = \frac{R_2 V_{in}}{R_1 + R_2} \text{ V}$$


We can see that,

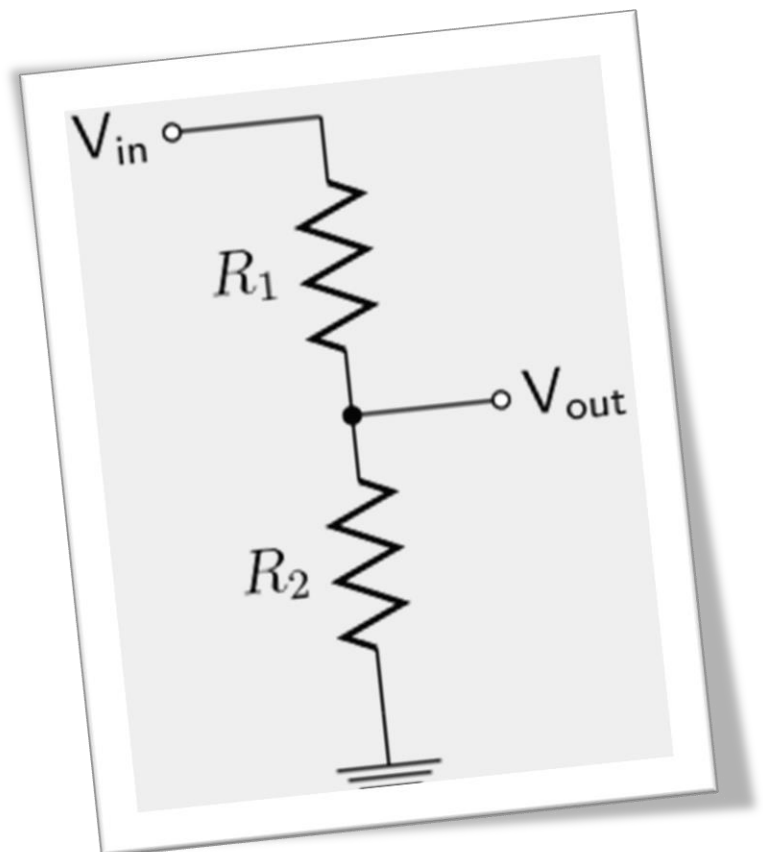We can get the output Voltage according to what we want by adjusting the values of Resistances.



Observations:

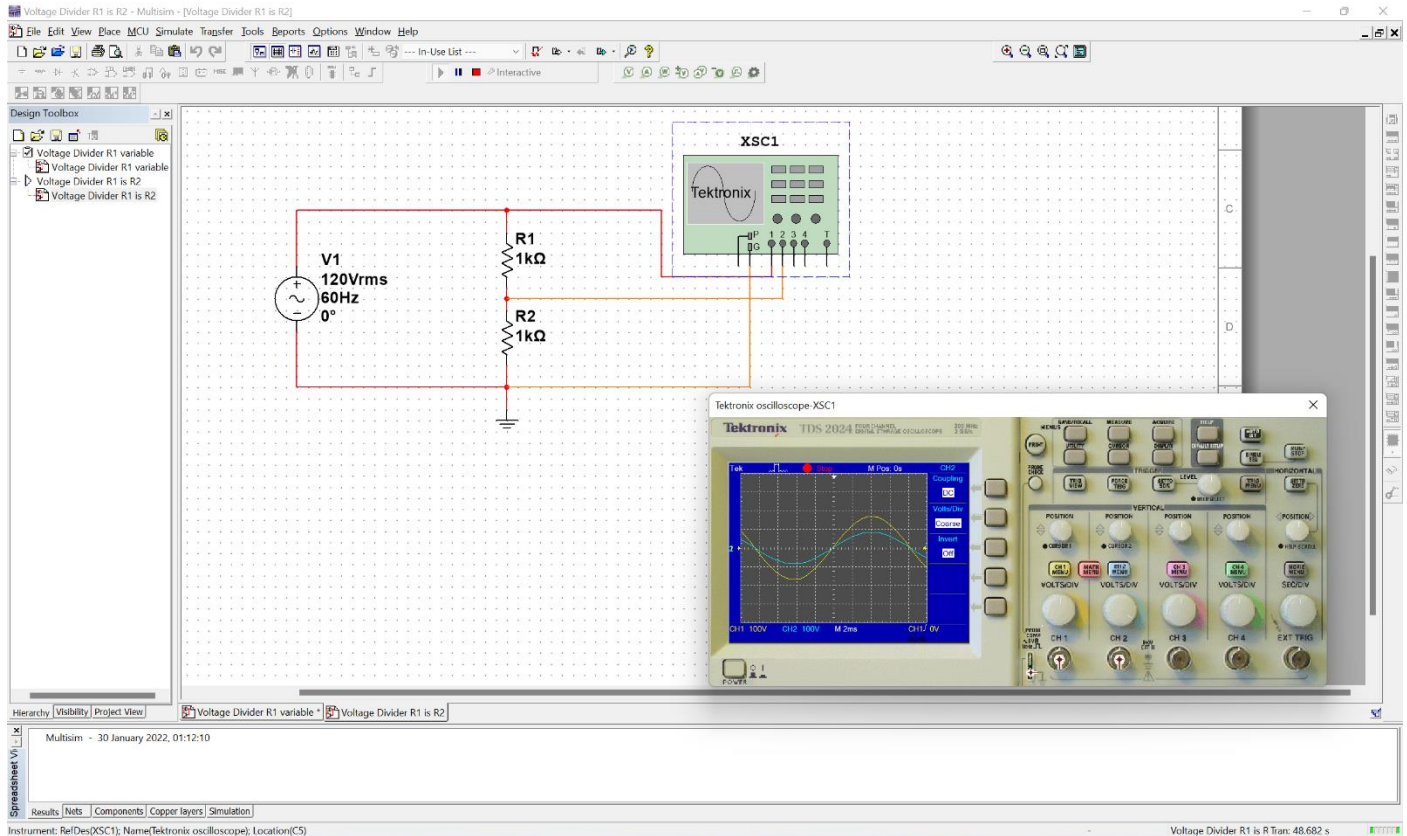Voltage Divider Circuit with $R_1 = R_2$ (Both Resistance Equal):



Using Tektronix oscilloscope, we will find out the voltage difference between R_2 and $R_1 + R_2$. The 2 waves at output corresponds the same.

To get the 2 waves we make the -ve terminal of the AC battery source as ground that is at Zero Volts (which is reference voltage).

As $R_1 = R_2$, so we get the 2nd wave with peak magnitude as half of the 1st one.

Equation for voltage here,

$$V = 120\sqrt{2} \sin(120\pi t) \text{ V}$$

$$R_1 = 1k \text{ ohm}$$

$$R_2 = 1k \text{ ohm}$$

Equation for the current in the circuit,

$$i = 60\sqrt{2} \sin(120\pi t) \times 10^{-3} \text{ A}$$

Equation for the Yellow Wave,

$$V_Y = i \times R = 120\sqrt{2} \sin(120\pi t) \text{ V}$$

Equation for the Blue Wave,


$$V_B = i \times R = 60\sqrt{2} \sin(120\pi t) \text{ V}$$

Voltage Divider Circuit with R1 Variable and R2 Fixed:

Using Tektronix oscilloscope, we will find out the voltage difference between R2 and R1+R2. The 2 waves at output corresponds the same.

To get the 2 waves we make the -ve terminal of the AC battery source as ground that is at Zero Volts (which is reference voltage).

Case I (R1 = 10% R2):

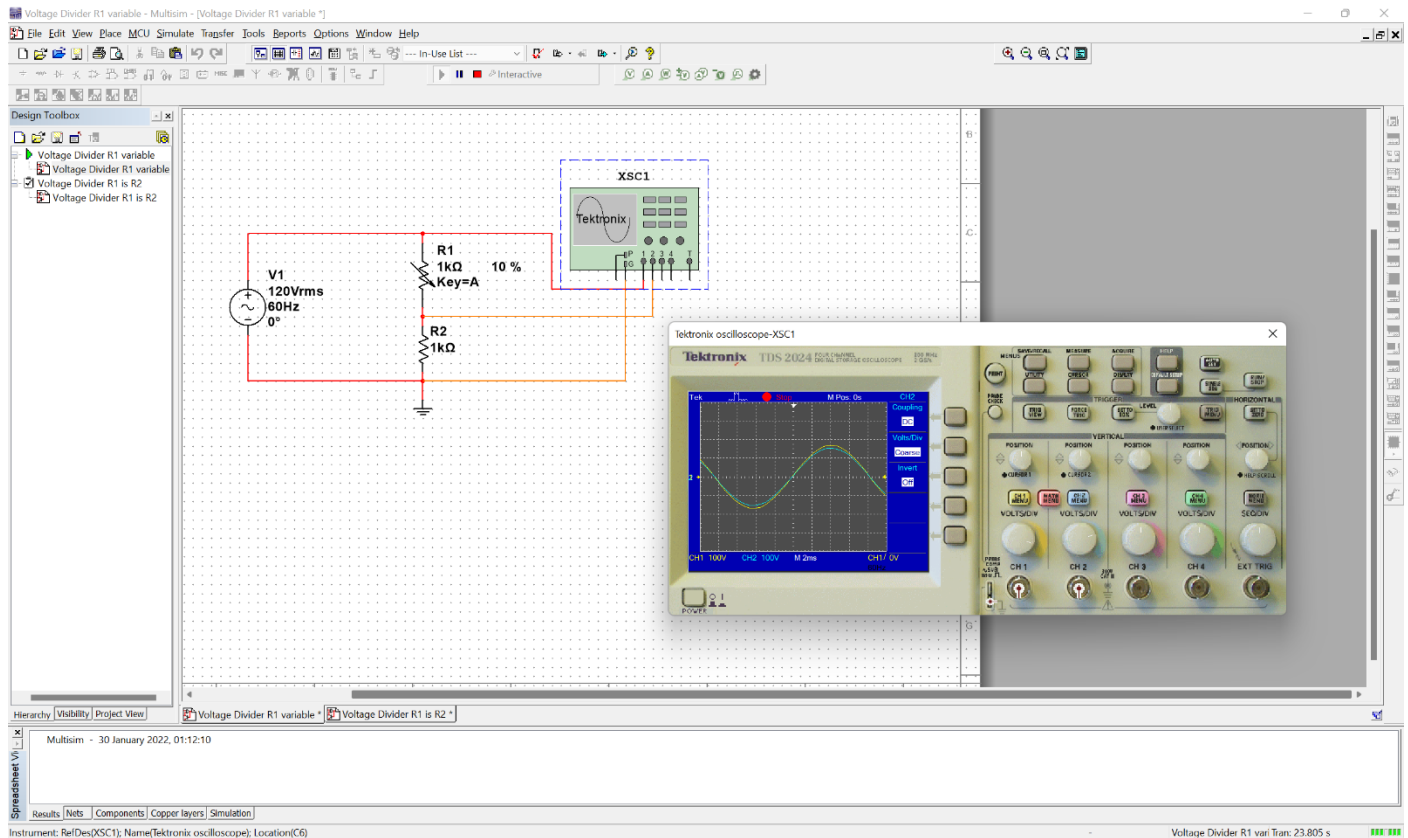

As $R1 = 10\%$ of $R2$, so we get the 2nd wave with peak magnitude closer to 1st wave as value of resistance is much low.

Equation for voltage here,

$$V = 120\sqrt{2} \sin(120\pi t) \text{ V}$$

$$R2 = 1k \text{ ohm}$$

$$R1 = 10\% \text{ of } 1k = 100 \text{ ohm}$$

Equation for the current in the circuit,

$$i = (10.91)\sqrt{2} \sin(120\pi t) \times 10^{-2} \text{ A}$$


Equation for the Yellow Wave,

$$V_Y = i \times R = 120\sqrt{2} \sin(120\pi t) \text{ V}$$

Equation for the Blue Wave,

$$V_B = i \times R = (109.1)\sqrt{2} \sin(120\pi t) \text{ V}$$

Case II (R1 = 50% R2):

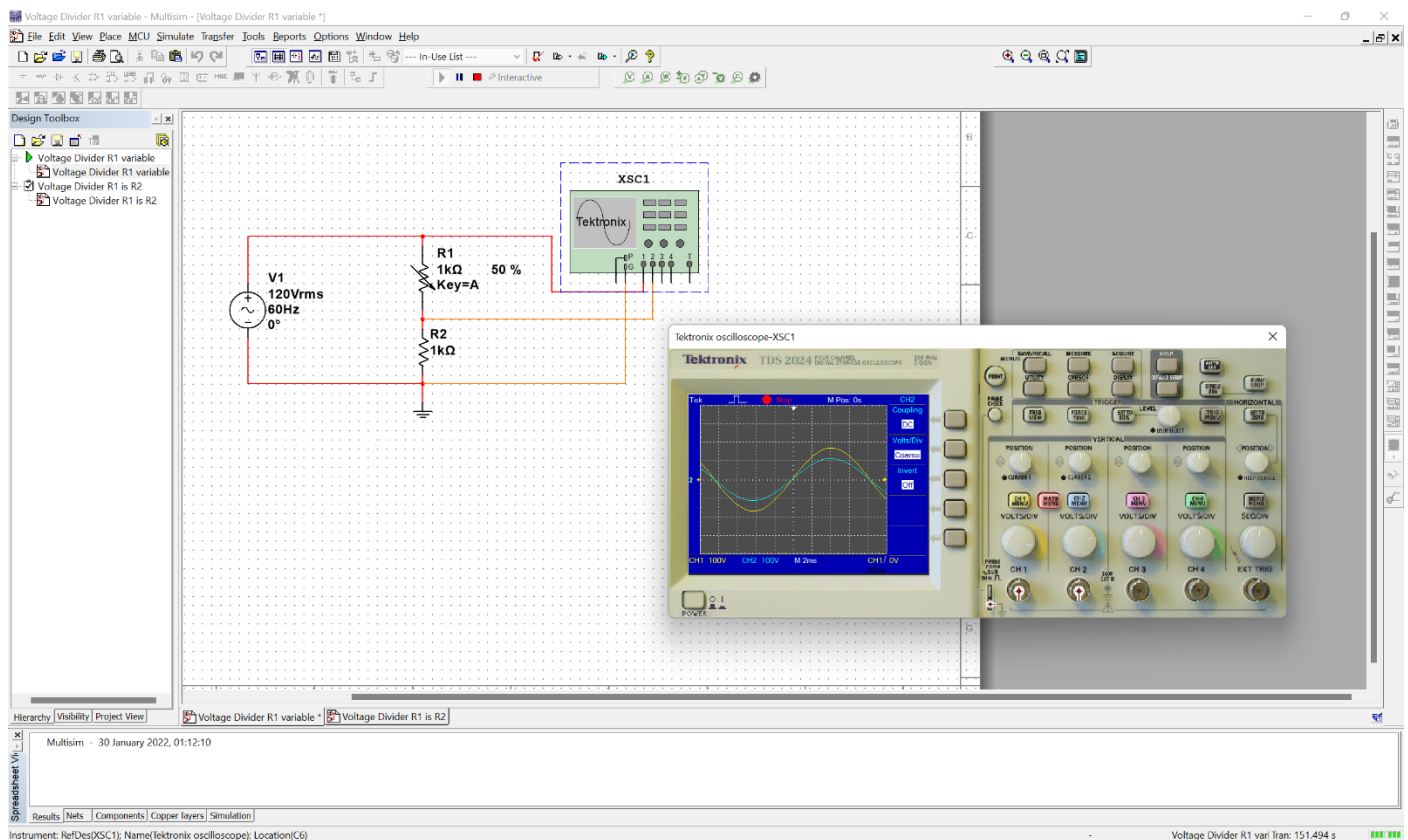

As $R1 = 50\%$ of $R2$, so we get the 2nd wave with peak magnitude away from 1st wave as compared to case I because value of resistance is increases.

Equation for voltage here,

$$V = 120\sqrt{2} \sin(120\pi t) V$$

$$R2 = 1k \text{ ohm}$$

$$R1 = 50\% \text{ of } 1k = 500 \text{ ohm}$$

Equation for the current in the circuit,

$$i = 8\sqrt{2} \sin(120\pi t) \times 10^{-2} A$$


Equation for the Yellow Wave,

$$V_Y = i \times R = 120\sqrt{2} \sin(120\pi t) V$$

Equation for the Blue Wave,

$$V_B = i \times R = 80\sqrt{2} \sin(120\pi t) V$$

Case III (R1 = 90% R2):

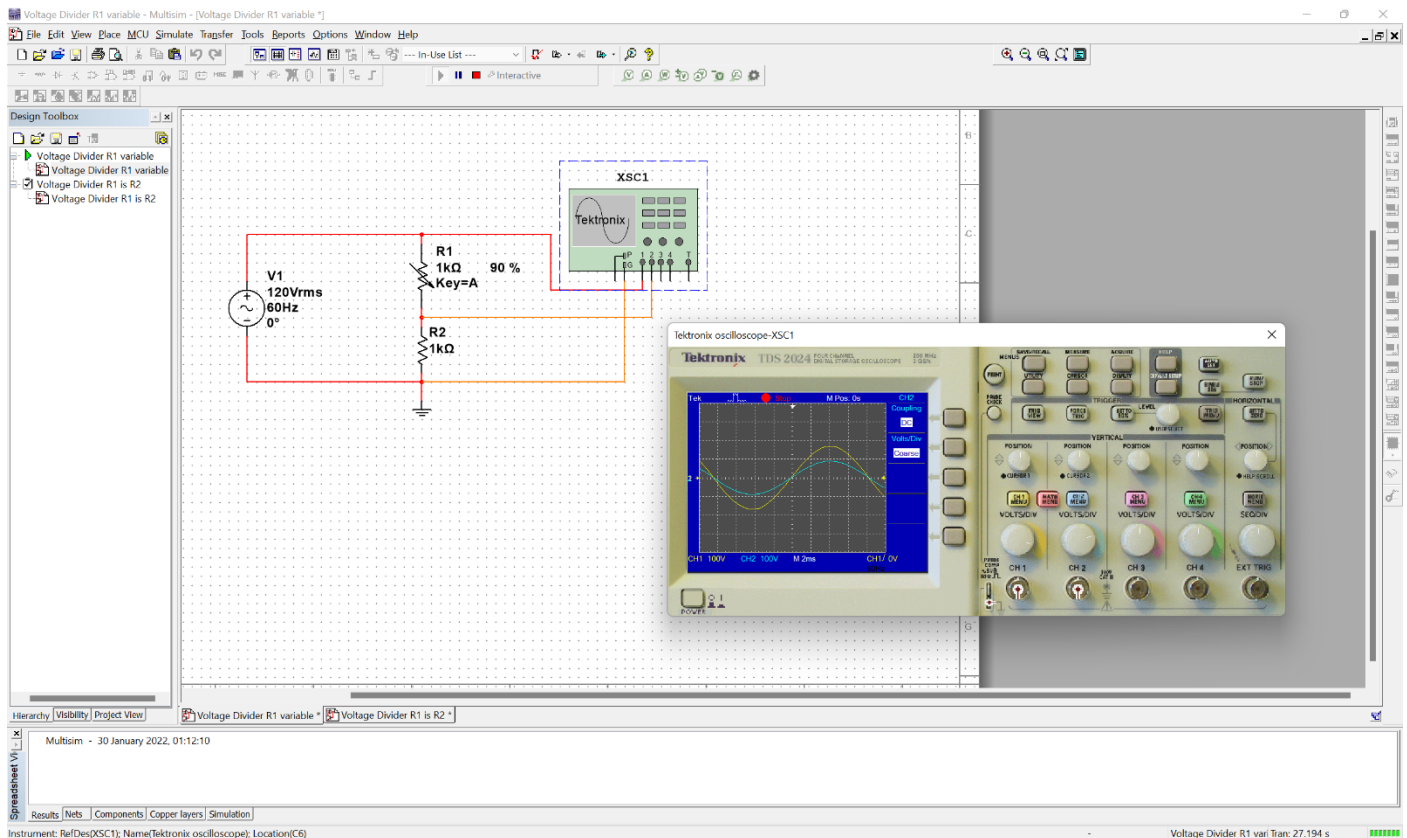

As $R1 = 50\%$ of $R2$, so we get the 2nd wave with peak magnitude away from 1st wave as compared to case II because value of resistance is increases.

Equation for voltage here,

$$V = 120\sqrt{2} \sin(120\pi t) V$$

$$R2 = 1k \text{ ohm}$$

$$R1 = 90\% \text{ of } 1k = 900 \text{ ohm}$$

Equation for the current in the circuit,

$$i = (6.31579)\sqrt{2} \sin(120\pi t) \times 10^{-2} A$$

Equation for the Yellow Wave,

$$V_Y = i \times R = 120\sqrt{2} \sin(120\pi t) V$$

Equation for the Blue Wave,

$$V_B = i \times R = (63.1579)\sqrt{2} \sin(120\pi t) V$$